

# Metastability & Synchronizers

In Digital Systems

# What Is Metastability?

- > Metastability occurs in a bistable (flip-flop or latch) circuit when, due to a setup/hold timing violation, the circuit is driven to an unstable equilibrium.
- > If the input changes right around the clock edge such that setup or hold time is violated, the flip-flop may be forced into that metastable region.
- > The metastable output is analog / indeterminate (floating between thresholds) and not valid logic until it resolves.
- > Over time (in nanoseconds to picoseconds), it decays (due to internal feedback) toward a valid logic level (0 or 1), influenced by noise or device imbalance.




# Metastability Probability Model

> Equation :

$$P(T > t) = e^{-\frac{t}{\tau}}$$

Where,

 - >  $P(T > t)$  = Probability that the flip-flop remains in the metastable state beyond time  $t$ .
- >  $\tau$  = Time constant of the flip-flop (characteristic decay time)
- > If you allow sufficiently large  $t$  (e.g. one or more clock cycles),  $P(T > t)$  becomes vanishingly small provides practical immunity to metastability.






# Metastability Probability Model


$$\text{MTBF} = \frac{1}{\text{failure rate}} = \frac{e^{S/\tau}}{T_W F_C F_D}$$

Where,

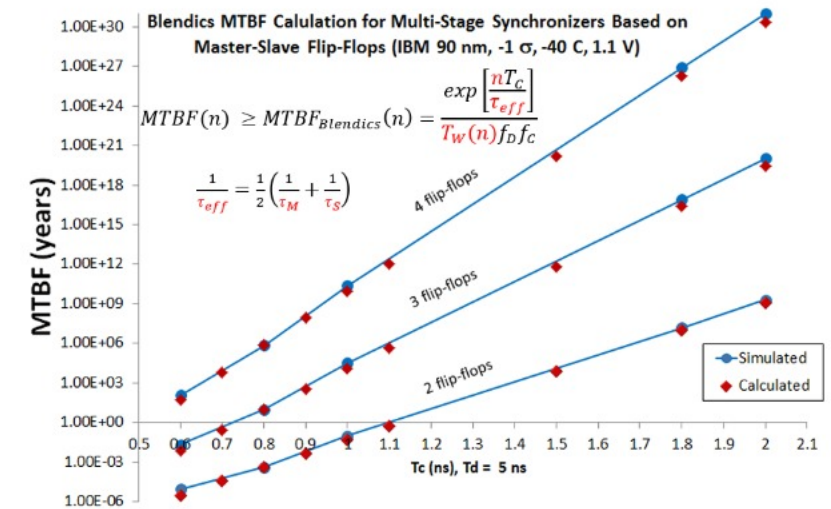- $T_W$  = Synchronization window (the vulnerable time window)
- $F_C$  = Clock frequency of the synchronizer (destination clock)
- $F_D$  = Data toggle rate (rate at which input changes)
- $S$  = Available settling time (slack time)
- $\tau$  = Time constant of the flip-flop
- Using 2-FF or 3-FF synchronizer effectively increases  $S$ , thus boosting MTBF massively.




# Double Flip-Flop Synchronizer

 

- > FF1 may go metastable if async input toggles near clock edge.
- > FF2 samples FF1's output one cycle later, after metastability has (with very high probability) resolved.
- > Adds 1 cycle latency but produces stable output.
- > Widely used in clock domain crossing (CDC) for single-bit signals.




# Double Flip-Flop Synchronizer

 


- Mathematical Impact:
  - Settling Time :  $S_{2FF} \approx S_{1FF} + T_{clk}$
  - MTBF Improvement :  $\frac{MTBF_{2FF}}{MTBF_{1FF}} = e^{T_{clk}/\tau}$

# Double Flip-Flop Synchronizer

 

- > FF1 may go metastable.
- > FF2 provides first resolution cycle, FF3 provides second resolution cycle.
- > Logic only uses FF3 output.
- > Adds 2 cycle latency, but makes metastability failure probability astronomically low.

# Double Flip-Flop Synchronizer

 


- Mathematical Impact:
  - Settling Time :  $S_{3FF} \approx S_{1FF} + 2T_{clk}$
  - MTBF Improvement :  $\frac{MTBF_{3FF}}{MTBF_{2FF}} = e^{T_{clk}/\tau}$


 
# Waveform Illustration

- Metastability cannot be eliminated, but it decays exponentially with time.
- FF1 may output uncertain values for a short time.
- FF2 gives one full clock cycle for metastability to resolve → stable output.



# Multi-bit Transfers

Problem with Multi-bit Clock Domain Crossing (CDC):

- Simple synchronizer (2-FF) works for single-bit signals.
- For multi-bit buses, synchronizing each bit independently may cause data corruption:
  - Bits may resolve at different times.
  - Receiver may sample a mixed / invalid word.
- Solutions:
  - Asynchronous FIFO
  - Handshake Protocols
  - Encoder Schemes (Gray Code)

# Design Guidelines for Handling Metastability & CDC

For Single-Bit Signals:

- Use 2-FF synchronizer (3-FF if ultra-critical).
- Keep synchronizer FFs physically close (to reduce routing delay).

For Multi-Bit Signals:

- Do not synchronize each bit separately.
- Use asynchronous FIFOs, handshake protocols, or Gray coding.
- Ensure atomic transfer of full data words.